

SMT. INDIRA GANDHI COLLEGE OF ENGINEERING

FE DEPARTMENT

SEM: I

SUB: BEE

BRANCH: ALL

TIME: 1 HOUR

MARKS: 20


Note: (1) Question No. 1 is compulsory.

(2) Attempt any three from remaining Questions.

Q1 A. State and explain maximum power transfer theorem. (3)

B. Using source transformation, convert the circuit given below to a single voltage source (2)


In series with a resistor.

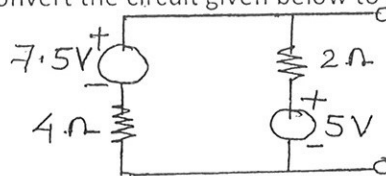


Q2. Calculate R_{XY} for the circuit shown in figure. (5)



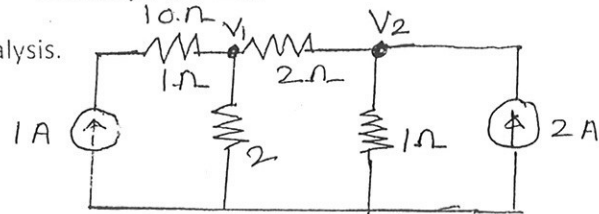
Q3. Find the voltage V_1 and V_2 using Nodal analysis. (5)



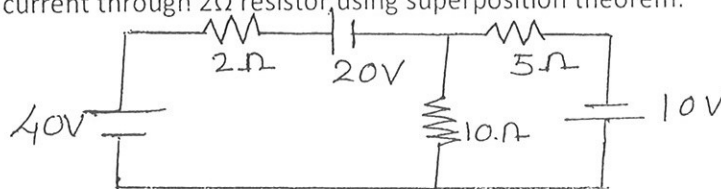Q4. Find the current through 2Ω resistor, using superposition theorem. (5)



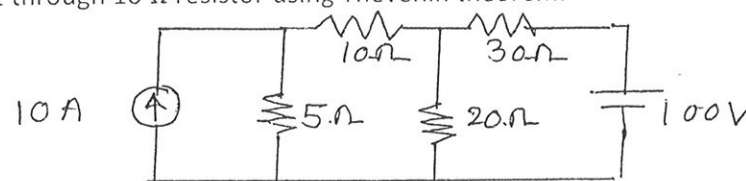Q5. Find the current through 10Ω resistor using Thevenin theorem. (5)



Q6. Find the average and RMS value of the waveform. (5)

