



PILLAI INSTITUTE OF INFORMATION TECHNOLOGY, ENGINEERING, MEDIA STUDIES & RESEARCH

NEW PANVEL - 410 206

UNIT TEST 1

SUBJECT: BEEE

DATE and TIME: 20/09/2014, 08:30 am

TOTAL MARKS: 20

DURATION: 1 HOUR

Q. 1. Solve any five. (Each question carries 2 marks)

(10 M)

- a) Thevenin's equivalent resistance R_{TH} for the network shown in the given figure is known to be 2Ω . Evaluate R .

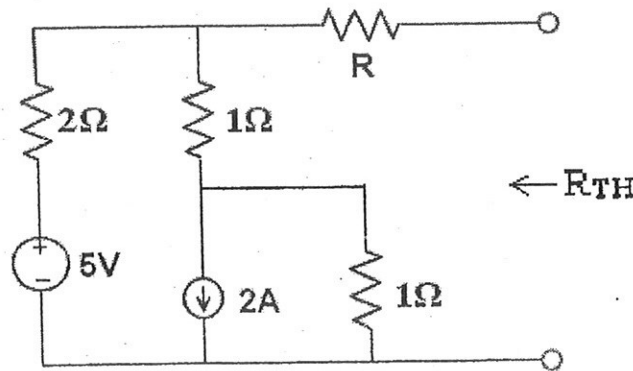


Figure 1.

- b) State and explain maximum power transfer theorem
- c) Find the current flowing through the ammeter for the given circuit.

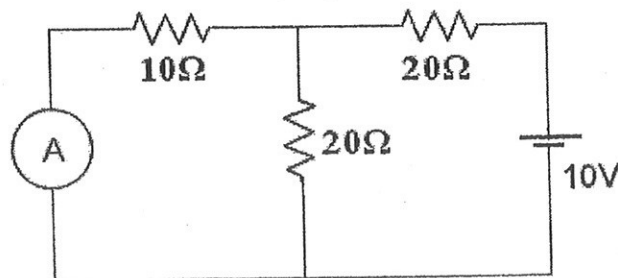


Figure 2.

d) Modify the circuit into one source and resistance to the left of points A and B.

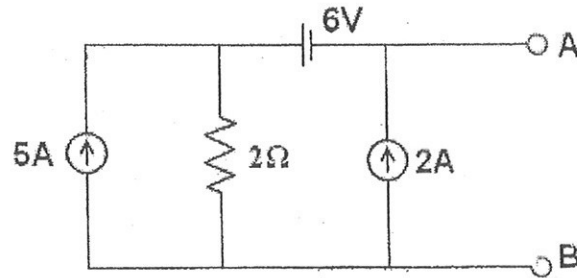


Figure 3.

e) Estimate the value of resistance between A and B.

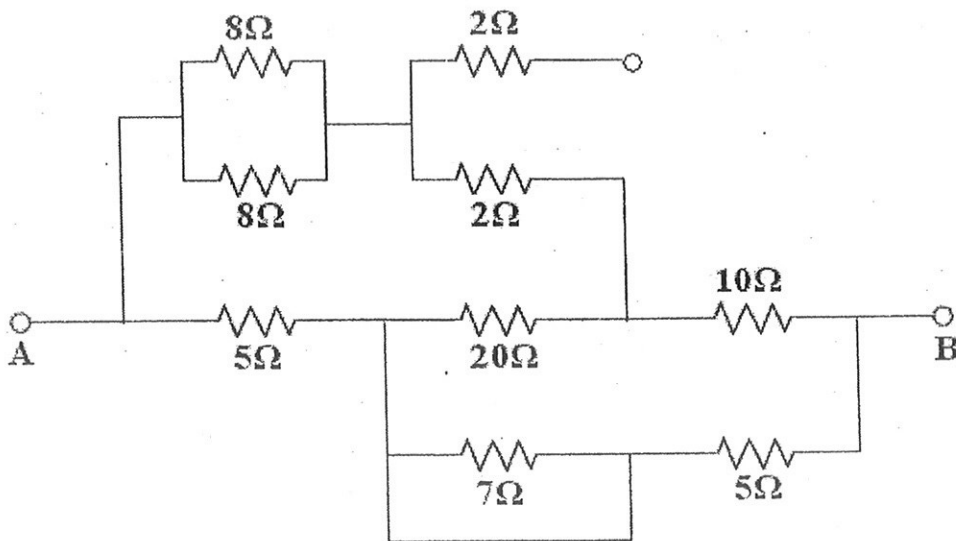


Figure 4.

f) Evaluate the current flowing in branch XY.

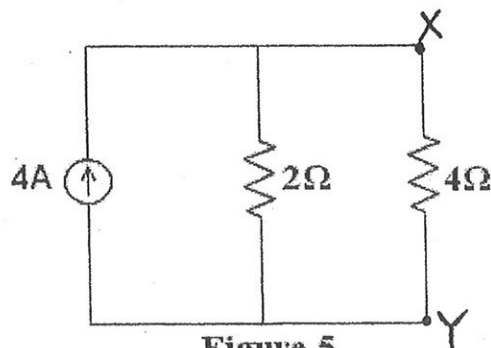


Figure 5.

Q.2.

- a) Compute the current in 15Ω resistance using Thevenin's theorem. (5M)

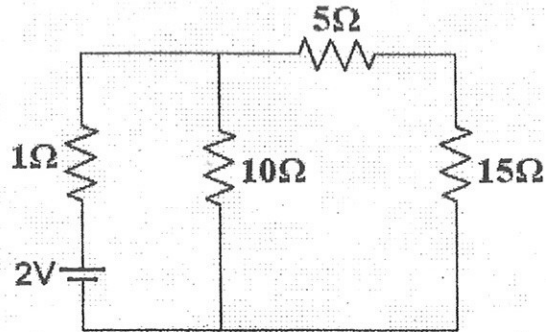


Figure 6.

Or

- b) For the network given below find the current through 3Ω resistor using Nodal analysis (5 M)

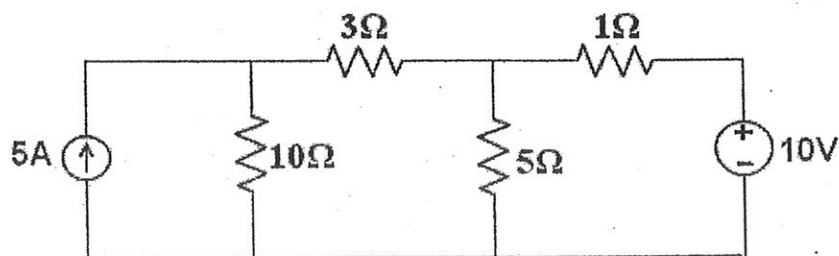


Figure 7.

Q. 3.

- a) Compute the current in 1Ω resistor using Superposition theorem. (5M)

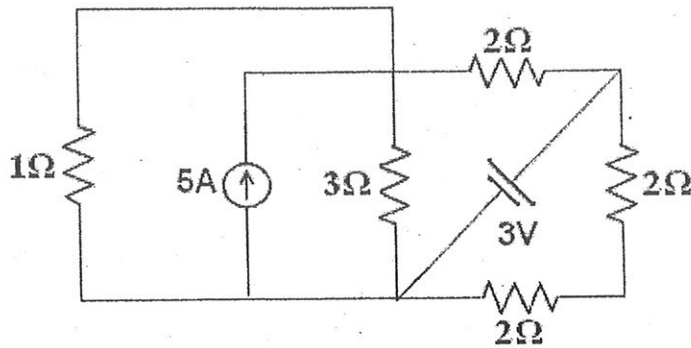


Figure 8.

Or

- b) Develop Norton's equivalent circuit across A and B. (5M)

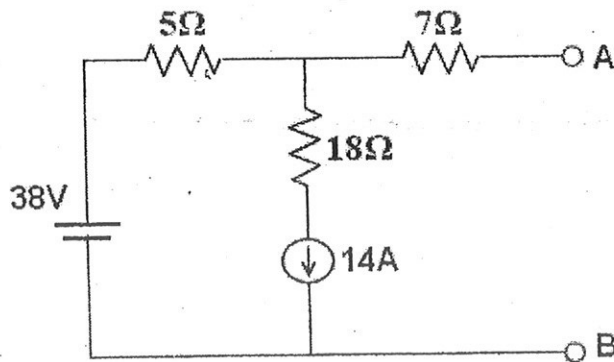


Figure 9.