


INTERNAL ASSESSMENT TEST NO.1
FE/SEM I /ALL DIV /BEE/ 13-09-2014/ MARKS 20

NB: Solve All Questions.

Figures to right shows full marks.


Q.1 Solve any five out of six questions.

10

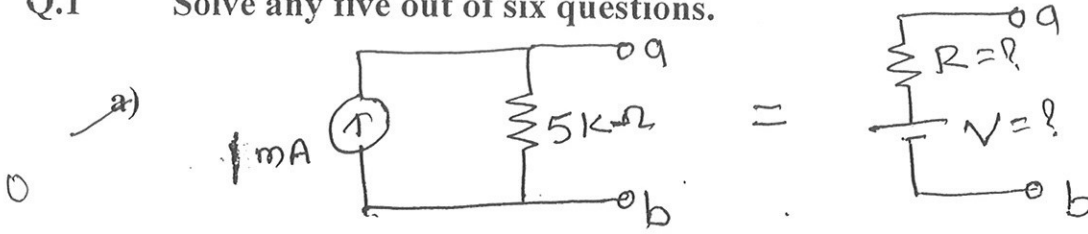


- I) 5mV, 5 Ω II) 5V, 5 KΩ III) 5V, 5 Ω IV) 5mV, 5K Ω

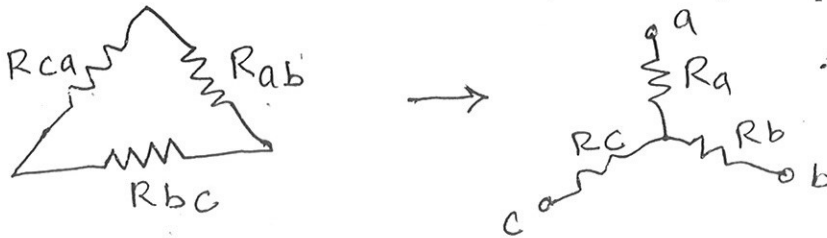b) If R_{ab} , R_{bc} and R_{ca} are connected in delta, then the R_b in equivalent star is



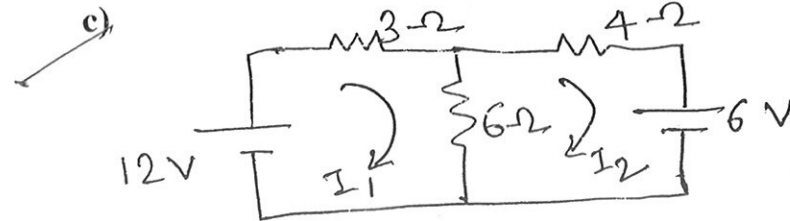
- I) $\frac{R_{ab} R_{bc}}{R_{ab} + R_{bc} + R_{ca}}$ II) $\frac{R_{ca} R_{bc}}{R_{ab} + R_{bc} + R_{ca}}$ III) $\frac{R_{ab} R_{ca}}{R_{ab} R_{bc} R_{ca}}$ IV) $\frac{R_{ab} R_{bc}}{R_{ab} R_{bc} R_{ca}}$



The KVL equations of circuit are

- I) $-3I_1 + 2I_2 = 4$, $3I_1 + 5I_2 = 3$ III) $3I_1 - 2I_2 = 4$, $3I_1 - 5I_2 = 3$
 II) $3I_1 - 2I_2 = -4$, $-3I_1 - 5I_2 = -3$ IV) $3I_1 + 2I_2 = 4$, $3I_1 + 5I_2 = 3$

d) V_{ab} in the following circuit is

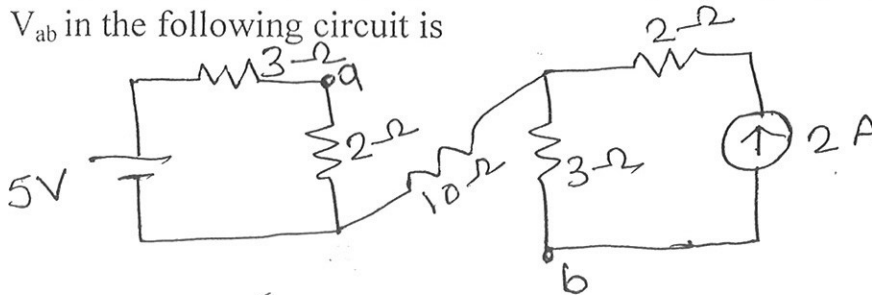


- I) -8V II) 8V III) 4V IV) 6V

e) Superposition Theorem can be applied to

- I) Linear, Unilateral III) NonLinear, Unilateral
 II) NonLinear, Bilateral IV) Linear, Bilateral

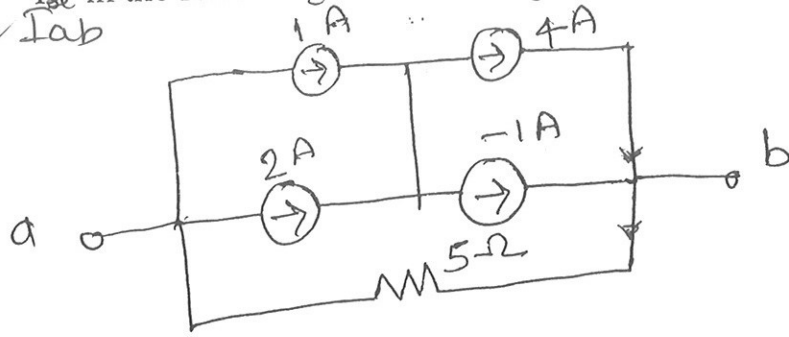Q.1 f) I_{bc} in the following network using Norton's Theorem will be




- I) 3A II) 6A III) 7A IV) 0


Q.2 a) Find R_{AB} .



OR b) Find V_1, V_2 By Nodal Analysis.

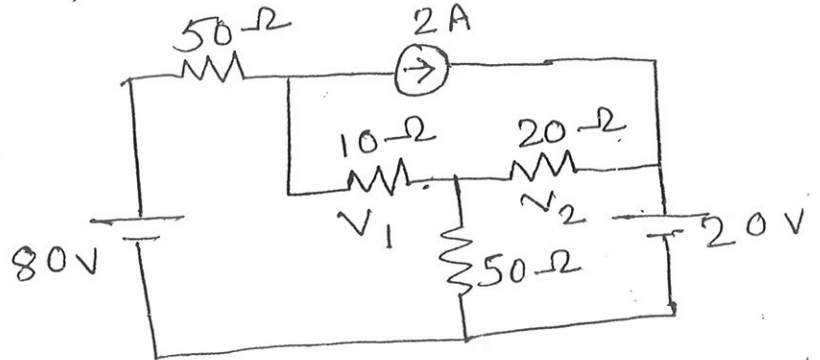

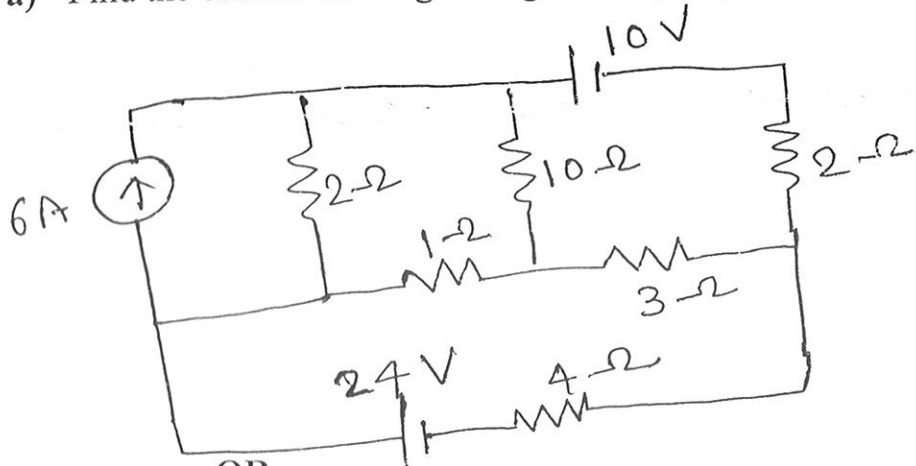Q.3 a) Find the current flowing through 4Ω by Superposition Theorem.



OR

b) Find R_L , if maximum power is transferred. Also find P_m .

