



TERM TEST-I

SUBJECT: BASIC ELECTRICAL AND ELECTRONICS ENGINEERING

YEAR/SEM: F.E. /I

DATE: 10/09/2014

BRANCH: All

TIME: 10am to 11 a.m.

MARKS: 20


- NOTE: 1) Question 1 is compulsory  
2) Attempt any 2 from Q2 to Q5

Q1) Multiple Choice Questions:-


(10M)

- 1) Mesh loop method of solving electrical network
  - a) Uses branch currents
  - b) Utilizes Kirchhoff's voltage law
  - c) is confined to single loop circuit method
  - d) is a network reduction method
- 1.2) Nodal method of circuit analysis is based on \_\_\_\_\_
  - a) KVL and Ohms law
  - b) KCL and Ohms law
  - c) KCL and KVL
  - d) KCL, KVL and Ohms law
- 1.3) Maximum power is delivered from source to load when the \_\_\_\_\_
  - a) when load resistance is equal to source resistance
  - b) when load resistance is short circuited
  - c) when both load and source resistance are different
  - d) when load resistance is open circuited
- 4) Find Max power transferred to load resistance in Thevenin equivalent circuit if  $R_{TH} = 10\Omega$  and  $V_{TH} = 10V$ .
  - a) 0.4 W
  - b) 0.25 W
  - c) 0.5 W
  - d) 2W
- 1.5) If there are 'n' nodes in any network, the number of simultaneous equations to be solved is
  - a) n
  - b) n+1
  - c) n-1
  - d)  $n^2$

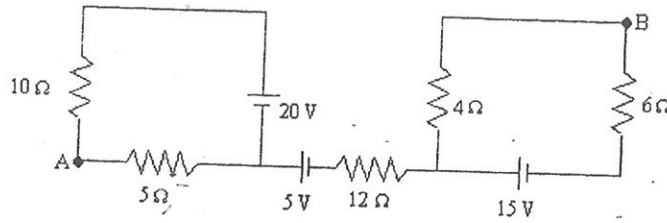
Q2) In the network shown, find the voltage between points A and B. (5M)



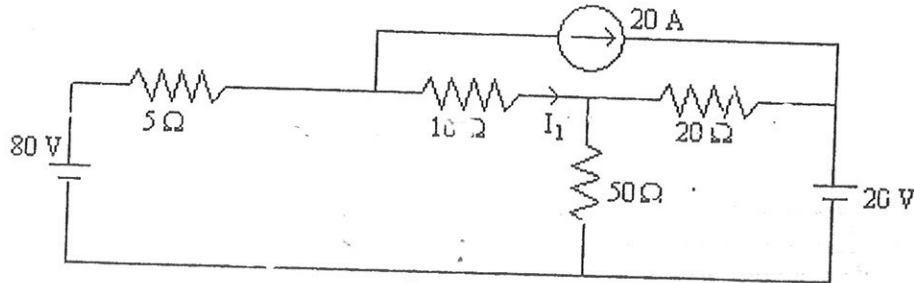Q3) Find current  $I_1$  by superposition theorem. (5M)



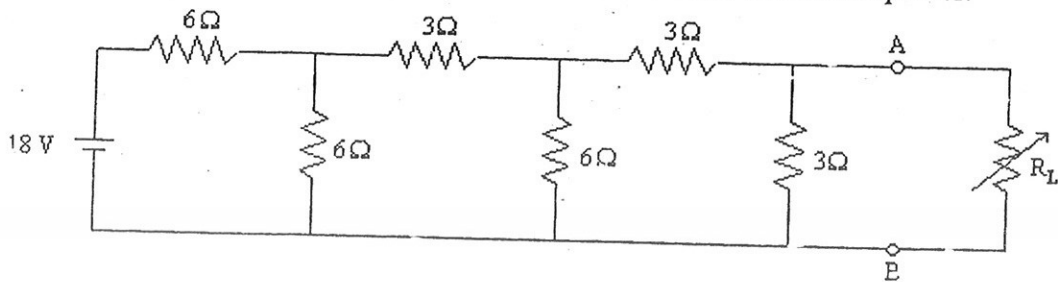Q4) Find value of  $R_L$  for maximum power transfer & calculate maximum power. (5M)



Q5) Find the current through 12 ohm resistor using nodal analysis. (5M)

