

V.E.S. INSTITUTE OF TECHNOLOGY, CHEMBUR

TEST I - SUBJECT BEE

DATE : 13/09/14


ODD NUMBERS

MAX MARKS:20


I Answer any FIVE :

(5*2=10)

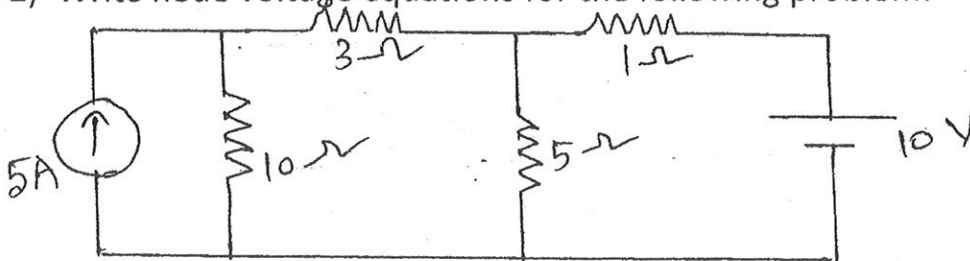
- 1) State maximum power transfer theorem.
- 2) Write node voltage equations for the following problem:



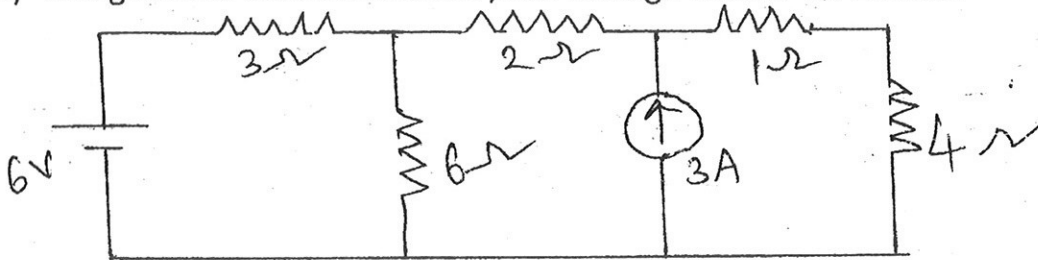
- 3) Using source transformation, find voltage across 4Ω resistor



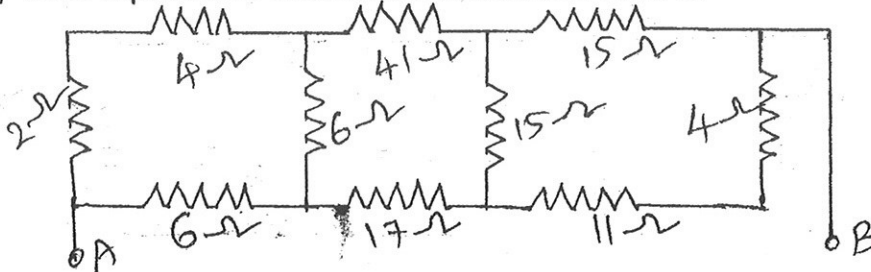- 4) Find equivalent resistance between A and B.




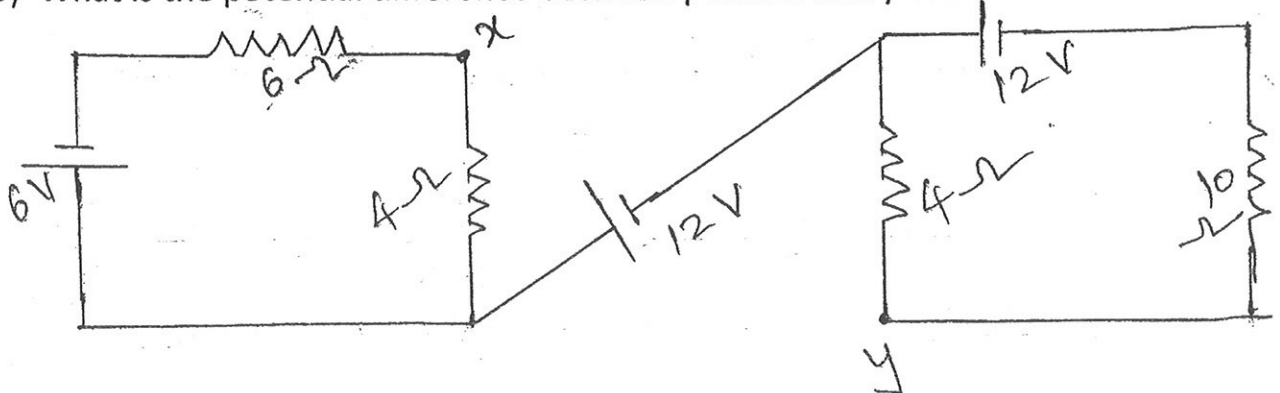- 5) What is the potential difference between points x and y in the network?




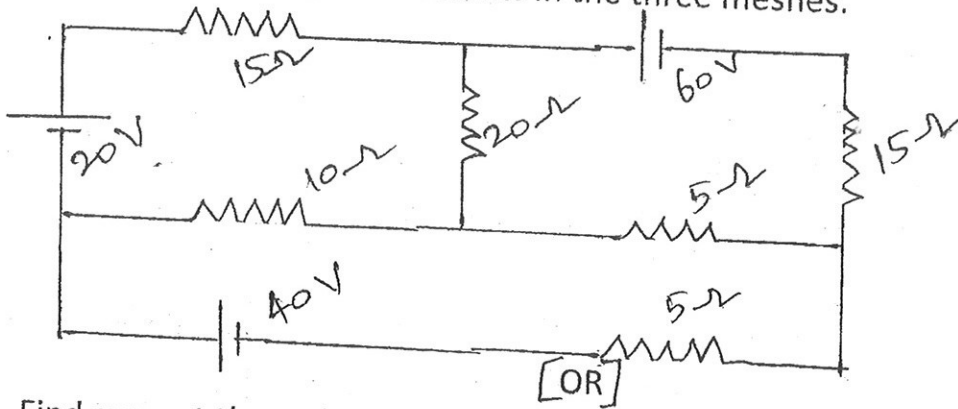6) A circuit consists of two parallel resistors, having resistances of $20\ \Omega$ and $30\ \Omega$ respectively, and is connected in series with a $15\ \Omega$ resistor. If the current through $15\ \Omega$ resistor is $3\ \text{A}$, find current through $20\ \Omega$ and $30\ \Omega$ resistors.


II Using mesh analysis, find currents in the three meshes. (5*1=5)



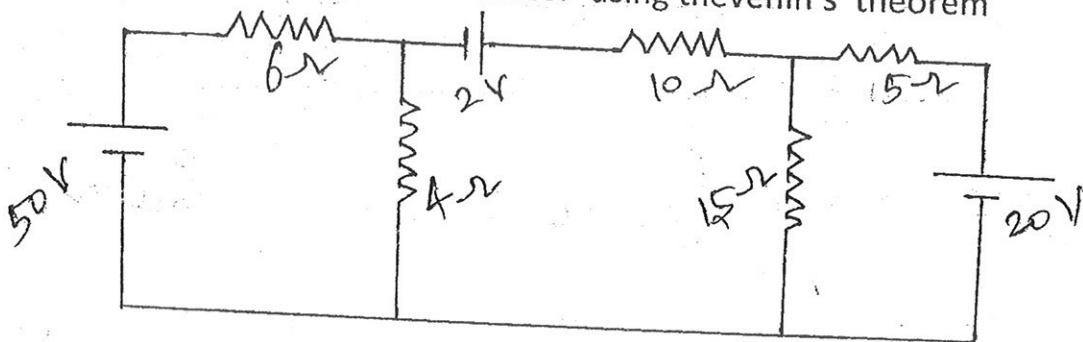Find current through $10\ \Omega$ resistor using thevenin's theorem



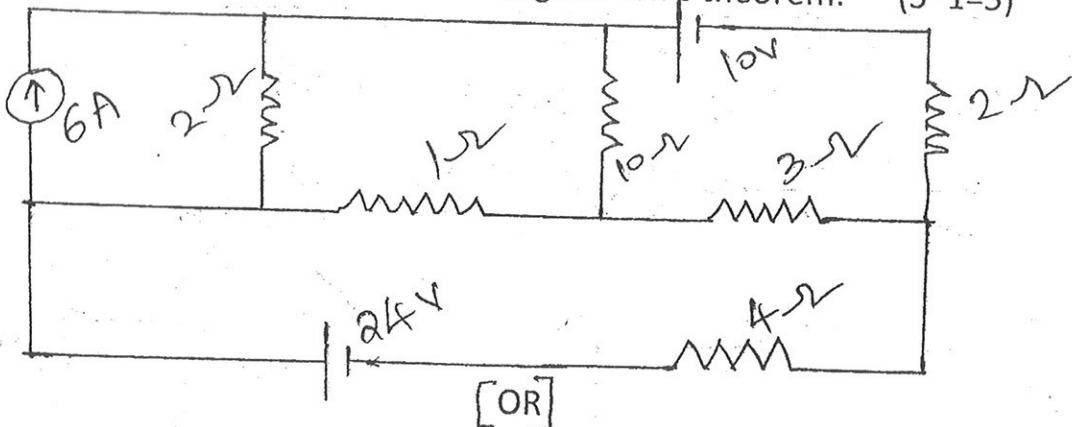III Find current through $4\ \Omega$ resistor using Norton's theorem. (5*1=5)



Find current in $5\ \Omega$ resistor by superposition theorem

