

TERNA ENGINEERING COLLEGE, NERUL
INTERNAL ASSESSMENT TEST-1

Class- FE (All)
 Date - 04/09/2015

Sub. - Basic Electrical and Electronics Engineering
 Time - 1 Hr.

Max. Marks - 20

Q1 Attempt any five.

2x5=10

- Equivalent resistance between points A & B for the network shown in fig. 1 is-
 (i) R (ii) 2R (iii) R/2 (iv) R/4
- KVL equation for mesh-1 in fig. 2 is-
 (i) $-2I_1 + I_2 = -2$ (ii) $2I_1 + I_2 = -2$ (iii) $2I_1 - I_2 = -2$ (iv) $-2I_1 + I_2 = 1$.
- Superposition theorem can be applied to-
 (i) Network with only one source (ii) Linear network (iii) Nonlinear network (iv) All of above.
- Norton's equivalent of the network shown in fig. 3, will have I_{SC} (or I_N) and R_i (or R_N) as-
 (i) 2A & 2 Ω (ii) 2A & 1 Ω (iii) 1A & 2 Ω (iv) 1A & 1 Ω .
- For maximum power transfer, the load resistance R_L should be -
 (i) Smaller than R_i (ii) Larger than R_i (iii) Equal to R_i (iv) 2 R_i .
- Internal resistance of ideal voltage source is-
 (i) Zero (ii) Infinity (iii) Anything between zero and infinity (iv) Cannot be predicted.

Q2 Attempt any one.

5x1=5

- Determine the current through 12 Ω for network shown in fig. 4 using source transformation.
- Determine the current through 10 Ω for network shown in fig. 5.

Q3 Attempt any one.

5x1=5

- Determine the current through 1 Ω for network shown in fig. 6 using superposition theorem.
- Find the value of R_L for maximum power transfer. Also find value of maximum power, for fig. 7.

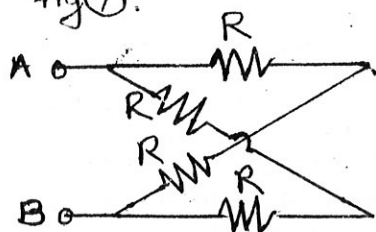


Fig.1 [Q-1(a)]

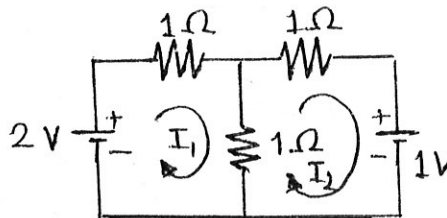


Fig.2 [Q-1(b)]

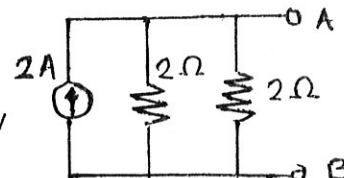


Fig.3 [Q-1(d)]

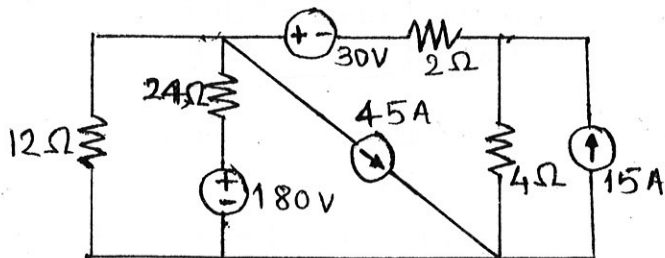


Fig. 4 [Q-2(a)]

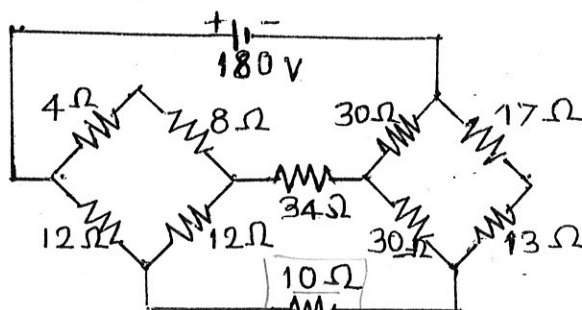


Fig.5 [Q-2(b)]

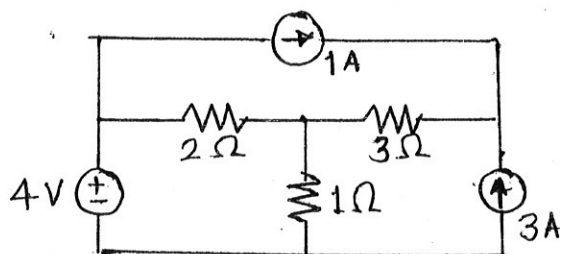


Fig. 6 [Q-3(a)]

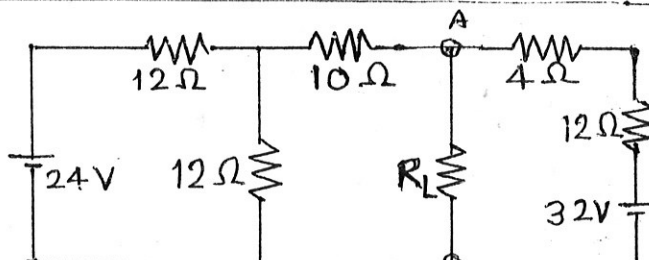


Fig. 7 [Q-3(b)]