



# Shah & Anchor Kutchhi Engineering College

Department: Electronics Engineering

Subject: BEE

Class: F.E


Marks: 20

Date: 28/10/2015


Duration: 60 Min.

**Q.1. Solve any five (Each 2 marks)**

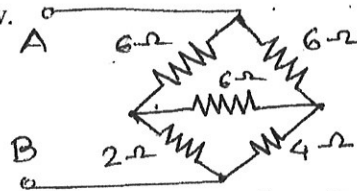- a) Write the expression for resonance frequency in a series RLC circuit and dynamic impedance in a parallel resonant circuit.
- b) Write the power equation for a three-phase circuit in terms of line values and phase values.
- c) Draw the phasor diagram for an ideal transformer under NO LOAD condition.
- d) State and explain Superposition Theorem.
- e) Find  $R_{AB}$  of circuit given below.



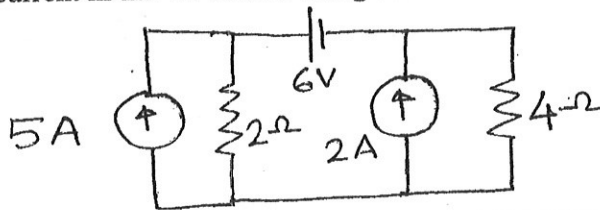- f) Find the current in the 4Ω resistor using source transformation.




- Q2 a)** Find the efficiency of the transformer of 230V / 115V, 50 Hz supply. If the watt meter in the open-circuit test reads a value of 0.03Watt and the watt-meter in short-circuit test reads 25Watt. If this transformer provides 75Watt to the load. (5 Marks)

OR

- Q2 b)** A choke coil of negligible resistance connected across a 500V, 50Hz supply takes 1A at 0.8pf. What capacitance must be placed in parallel with it in order to make the power factor of combination equal to unity. (5 Marks)

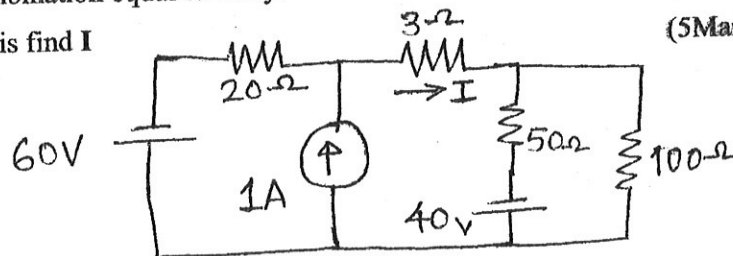- Q3 a)** Using Nodal Analysis find I (5Marks)



OR

- Q3 b)** Find value of  $R_L$  for Max. Power Transfer & Calculate Max. Power. (5Marks)

