

Vivekanand Education Society's Institute of Technology Internal Assessment II

Class: F.E.

Subject: B.E.E

ODD

Date:

Time:

Max Marks: 20

Note the following instructions.


1. All questions are compulsory.
2. Draw neat diagrams wherever necessary
3. Assume data, if missing, with justification.

Attempt any five out of six

Q.1

[2 x 5]

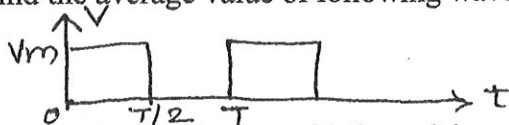- a) Define parallel resonance in ac circuit and write the equation of parallel resonant frequency.
- b) For series RLC circuit having $R=10\ \Omega$, $L=0.01\ \text{H}$ and $C=100\ \mu\text{F}$, find resonant frequency and quality factor.
- c) An alternating current I is given by $i=141.4\ \sin 314t$, find 1) peak value
2) time period
- d) Find the average value of following waveform




- e) Draw a phasor diagram of 3phase delta connected load.
- f) Three identical coils each $[4.2+5.6j]\ \Omega$ are connected in star across 415 V, 3phase 50 Hz supply. Determine 1) V_{ph} 2) I_{ph} 3) Power Factor

Q.2 a. Explain two Wattmeter method for the measurement of three phase power [5]

OR

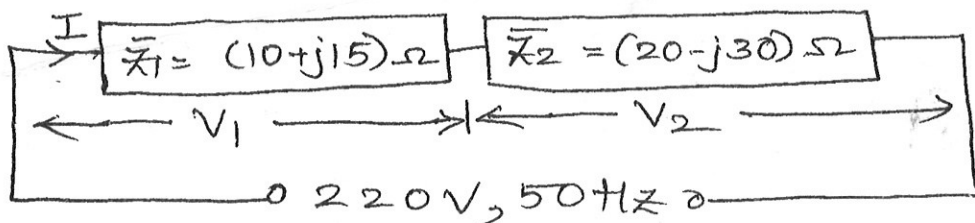b. For the circuit shown below, find current, V_1 & V_2 & Power factor [5]



Q.3 a. Three identical coils each with 15 ohms resistance & 0.03H of inductance are connected in delta to three phase 400V, 50Hz supply. Calculate phase current, line current & total power absorbed. [5]

b. Three sinusoidal voltages acting in series are given by $V_1=10\sin 440t$, $V_2=10\sqrt{2}\sin(440t-45^\circ)$, $V_3=20\cos 440t$ Derive the expression for the resultant voltage & determine the frequency & rms values of resultant voltages [5]